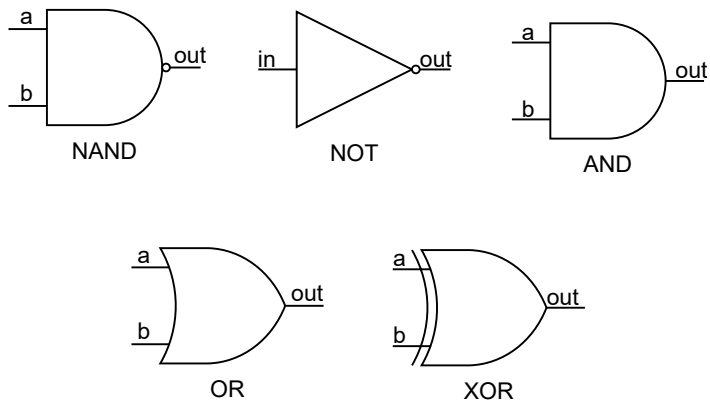


LEGEND:



Homework #1


CS220 - Computer Architecture + Machine Language

Author: Alexandra Burke

Section: 1319

Last Modified: 6/18/2023


NOT

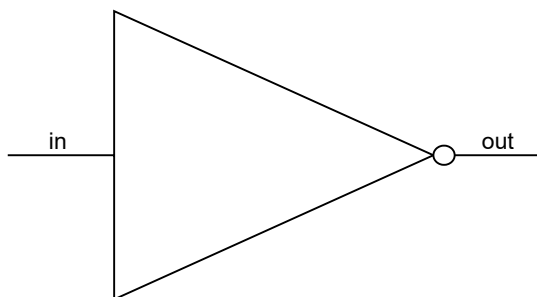

in	out
0	1
1	0

NOT: input is opposite of output


AND

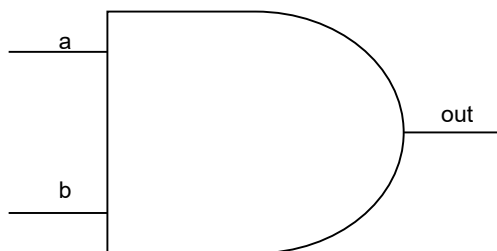

a	b	out
0	0	0
0	1	0
1	0	0
1	1	1

AND: only time output is positive is if all inputs are positive


OR

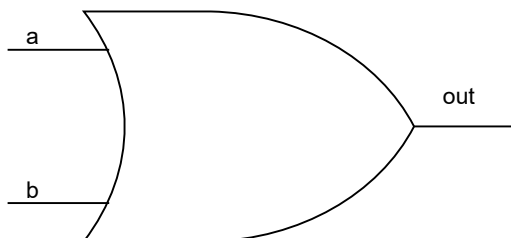

a	b	out
0	0	0
0	1	1
1	0	1
1	1	1

OR: output will be positive when any one or all inputs are positive

XOR

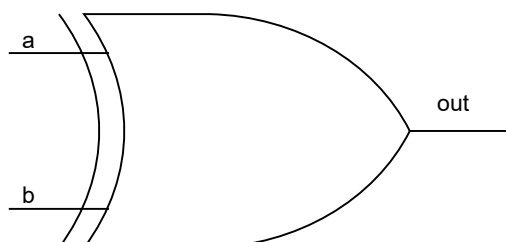

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

XOR: only positive when inputs not the same